

**COMPUTER AIDED ENGINEERING GRAPHICS  
TERM PROJECT**

**LEAD BATTERY LEVEL INDICATOR BOARD**

**PREPARED BY  
Omer Farouk MACHMOUTLAR  
05220000098**

**INSTRUCTOR  
Prof. Dr. Mutlu BOZTEPE**

**EGE UNIVERSITY  
Department of Electrical and Electronics Engineering  
IZMIR, 2024**

## PROJECT SUMMARY


With this circuit, we can see the remaining energy in a lead car battery through LEDs. This process is carried out with the integrated circuit named LM3914N. This IC is a monolithic integrated circuit that senses analog voltage levels and drives 10 LEDs, providing a linear analog display. The source of this project is a YouTube channel called (Creative Techos). After I decided to make the PCB with a CNC machine, it was quite difficult for me to learn how to use it. However, thanks to people in the Electrical Engineers chamber, I learned to use the CNC machine and printed the PCB successfully. While making this project, I had a hard time with the soldering part and I think that I did not solder the PCB in a right way. I will do a lot of soldering practice in my spare time.

## BOM LIST


Part	Value	Device
BATTERY J5	AK500/2	AK500/2 CONNECTOR
H1	MOUNT-HOLE3.0	MOUNT-HOLE3.0 3,0
H2	MOUNT-HOLE3.0	MOUNT-HOLE3.0 3,0
H3	MOUNT-HOLE3.0	MOUNT-HOLE3.0 3,0
H4	MOUNT-HOLE3.0	MOUNT-HOLE3.0 3,0
IC1	LM3915N	LM3915N DIL18 Dot/Bar Display Driver
JP1	pin 1	PINHD-1X1 1X01 PIN HEADER
JP2	pin2	PINHD-1X1 1X01 PIN HEADER
LED1	TLLR4400	LED3MM Low Current (2mA) LED 3 mm
LED2	TLLR4400	LED3MM Low Current (2mA) LED 3 mm
LED3	TLLR4400	LED3MM Low Current (2mA) LED 3 mm
LED4	TLLR4400	LED3MM Low Current (2mA) LED 3 mm
LED5	TLLR4400	LED3MM Low Current (2mA) LED 3 mm
LED6	TLLR4400	LED3MM Low Current (2mA) LED 3 mm
LED7	TLLR4400	LED3MM Low Current (2mA) LED 3 mm
LED8	TLLY4400	LED3MM Low Current (2mA) LED 3 mm
LED9	TLLG4400	LED3MM Low Current (2mA) LED 3 mm
LED10	TLLG4400	LED3MM Low Current (2mA) LED 3 mm
R1	56k	R-EU_0204/7 0204/7 RESISTOR
R2	4.7k	R-EU_0204/7 0204/7 RESISTOR
R3	18k	R-EU_0204/7 0204/7 RESISTOR
R4	10k	TRIM_EU-S64W S64W POTENTIOMETER



PRINTED CIRCUIT BOARD

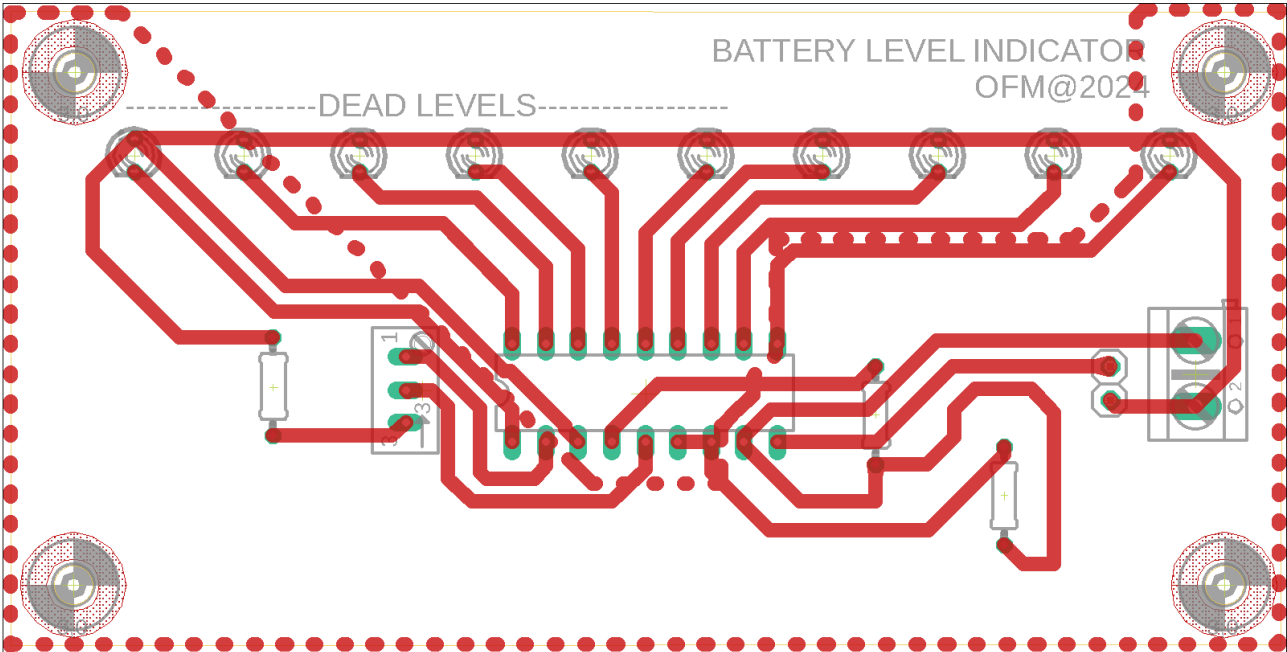


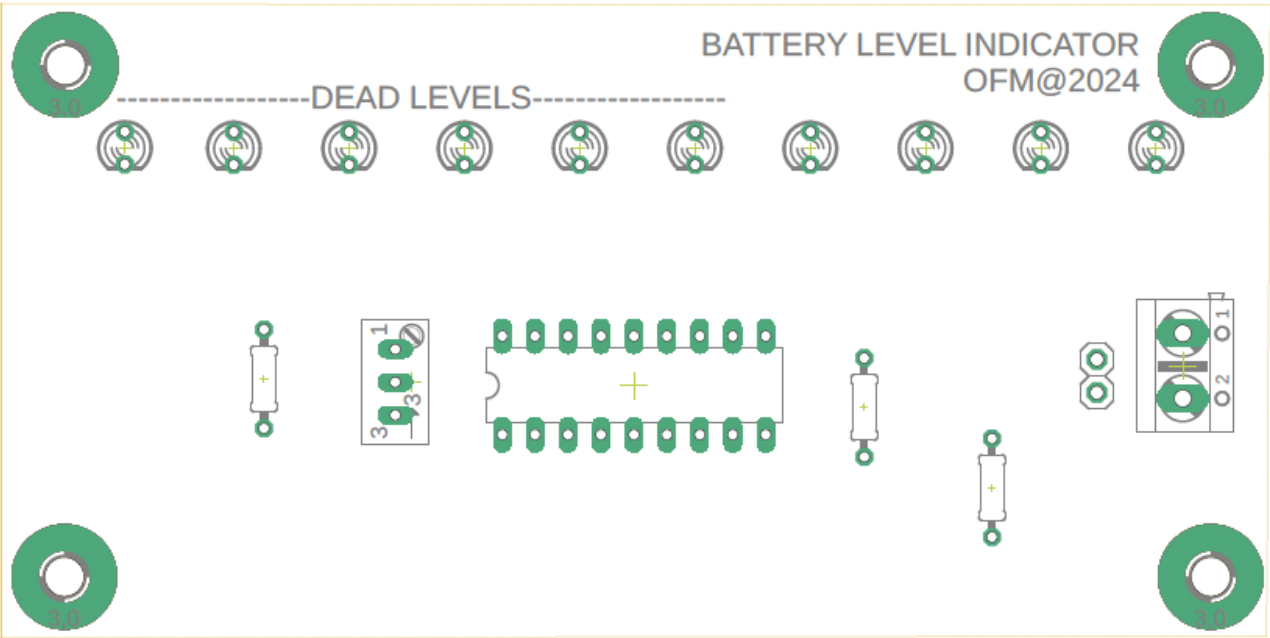Top view of the PCB(layer 1,17,21,22,23,24,25,26,51 and 52 are on)




Top view of the PCB (layer 17,21,23,25,26 and 51 are on)


### 3D VIEW OF THE PCB

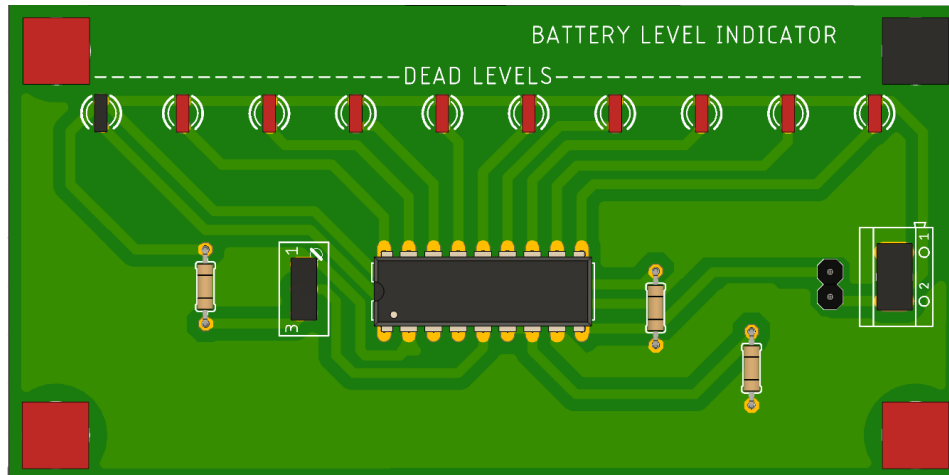

Top view of the PCB

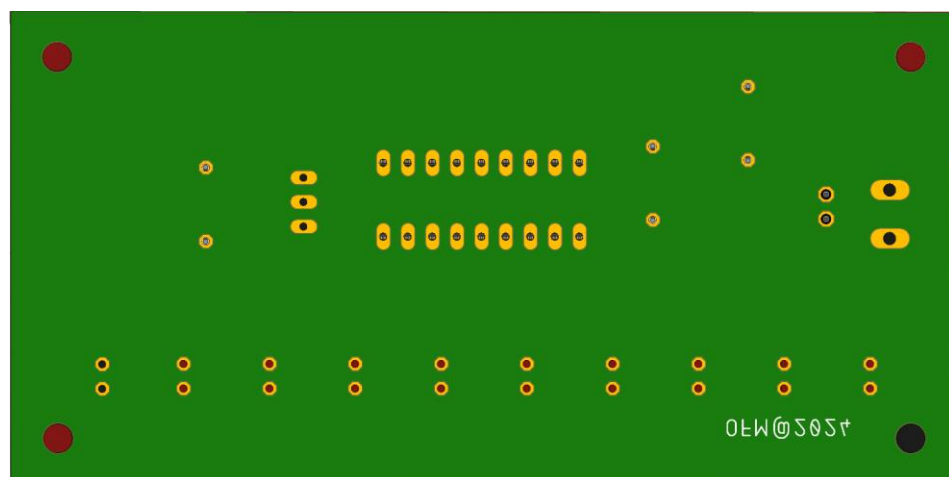


Bottom view of the PCB

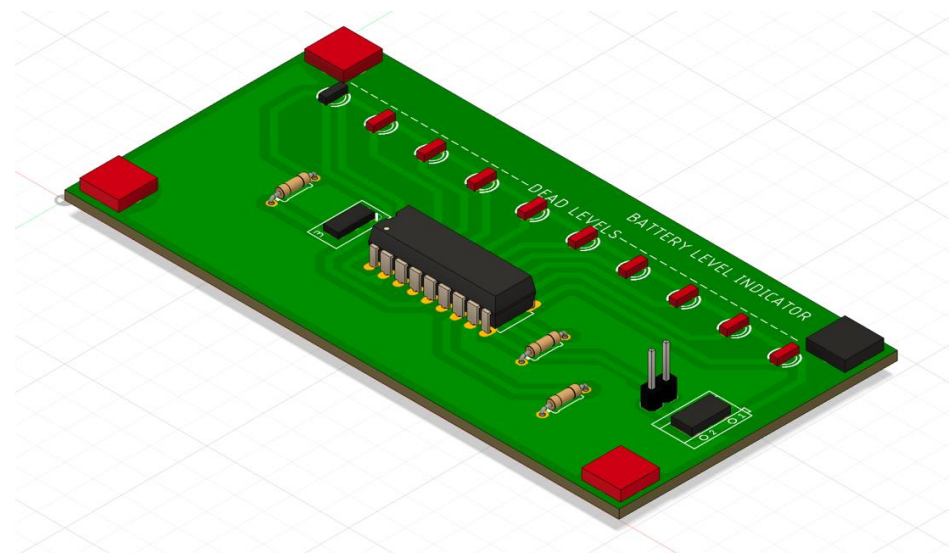


Isometric view of the PCB


## PHOTOGRAPHS OF THE PCB

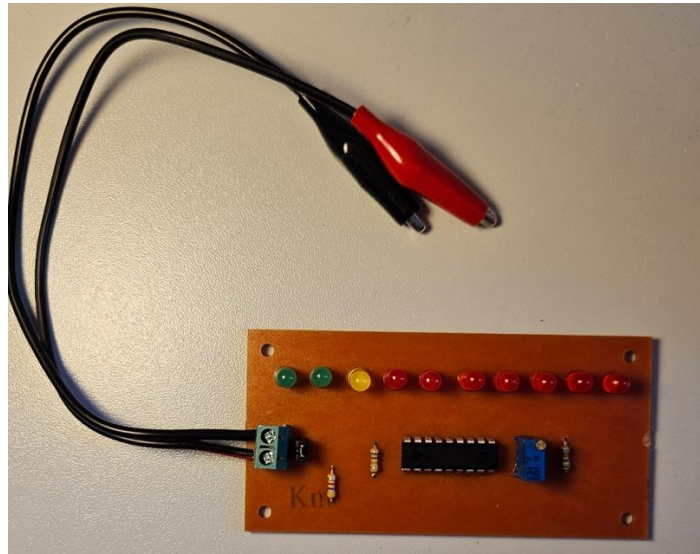

Top view of the PCB

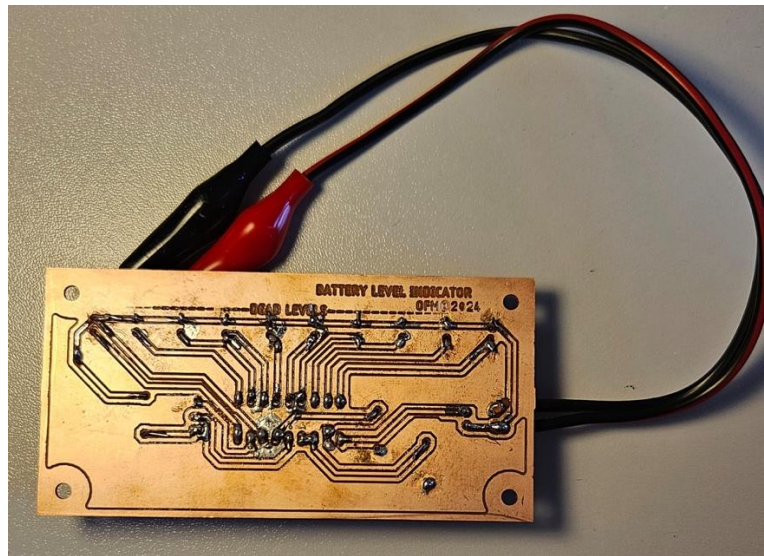

Bottom view of the PCB

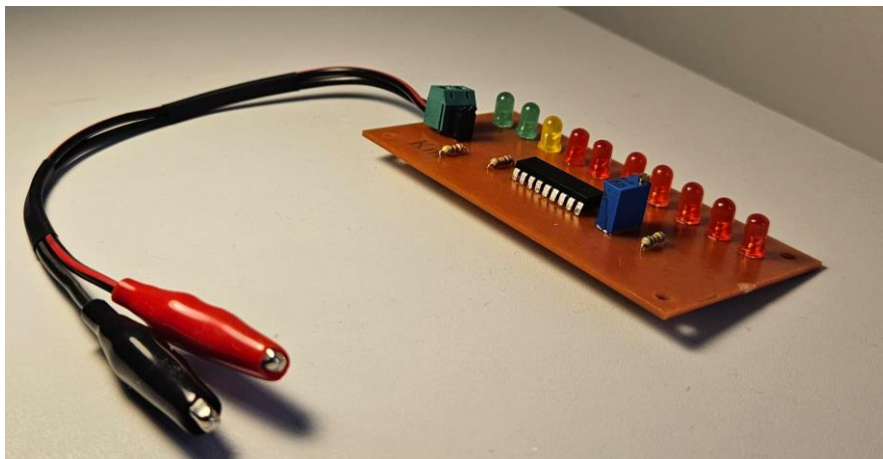

Isometric view of the PCB

## SOURCES

<https://www.youtube.com/watch?v=6A4N8pADOQw&t=1s>

<https://circuitdigest.com/electronic-circuits/simple-battery-level-indicator-using-op-amp>

<https://www.youtube.com/watch?v=ibZcQLibets>

<https://www.makerspaces.com/how-to-solder/>

[https://www.alldatasheet.com/view.jsp?Searchword=Lm3914n&gad\\_source=1&gclid=CjwKCAjwo6GyBhBwEiwAzQTmc\\_0cBryDsoxpXDOoszZrLjqg3vFuopOqTDqm-El8xXohEZHf4GFaxoCURYQAvD\\_BwE](https://www.alldatasheet.com/view.jsp?Searchword=Lm3914n&gad_source=1&gclid=CjwKCAjwo6GyBhBwEiwAzQTmc_0cBryDsoxpXDOoszZrLjqg3vFuopOqTDqm-El8xXohEZHf4GFaxoCURYQAvD_BwE)